

Register Number: 20322213026

C-6452

Name of the Candidate:

B.C.A. DEGREE EXAMINATION, DECEMBER 2022

(FOR AFFILIATED COLLEGES)

(NEW REGULATION 2022 ONWARDS)

COMPUTER APPLICATION

FIRST YEAR - I SEMESTER

22UBCAC14 DIGITAL COMPUTER FUNDAMENTALS

Time : 3 Hours

Maximum : 75 Marks

PART - A

10 x 2 = 20

Answer All Questions

1. List out various number systems ✓
2. Write the steps involved in conversion of binary-to-gray code conversion ✓
3. Visualize four variable K-map ✓
4. Show the truth table of NAND gate ✓
5. Draw the logic circuit for $X = AB + CDE$ ✓
6. Discuss the need of encoders ✓
7. State the significance of Hold time ✓
8. Show the logic circuit of clocked R-S Flip-Flop ✓
9. State the different types of modules available in SDRAM.
10. What do you mean by Worm?

PART - B

5 x 5 = 25

Answer All Questions

11. a) What is the equivalent octal and binary numbers for the given decimal number 498.25?

[OR]

- b) Discuss 1's complement subtraction with example.

12. a) Enumerate any Five laws of Boolean Algebra.

[OR]

- b) Write the following expression in simplified form using K-Map:
 $Y = \sum_m (3, 4, 5, 7, 9, 13, 14, 15)$

13. a) Identify the significance of 8 - to -1 multiplexers.

[OR]

- b) Construct BCD - to - Decimal decoder circuit and explain it.

14. a) Write a note on RS Flip-Flop.

[OR]

b) Write a note on bidirectional shift registers.

15. a) Write a note on Internal ROM organization.

[OR]

b) Discuss about FIFO memories.

PART - C

3 x 10 = 30

(Answer Any Three Questions)

16. Express the following:

(a) $10111.1011_2 = ?_{10}$

(b) $1024_8 = ?_2$

(c) $AB2_{16} = ?_8$

(d) $4163_8 = ?_{16}$

17. Represent DeMorgan's Law using logic gates.

18. Utilize the exclusive OR gate to build the parity generators and checkers.

19. Explain in detail about JK Flip-Flop.

20. Bring out the significance of magnetic and optical storage mechanisms.